 


# Power Integrity and Decoupling of **Fast** Integrated Circuits

AFCEM

 RF &  
Microwave



Yves Leduc,  
*Associate Member, Polytech'Lab,  
University of Nice Sophia-Antipolis  
Sophia-Antipolis*

Nathalie Messina,  
*Multimedia Function Architect & Feature Reference,  
Magneti Marelli Infotainment & Telematics,  
Sophia-Antipolis*

# Power Supply Impact on IC's Functionality

*How the power is supplied to an integrated circuit greatly affects the functionality of the system:*

- *External bypass capacitors cannot address the high frequencies issues [e.g. Fujitsu\_02].*



*Supplying power to high speed integrated circuits is a challenging task:*

- *$L di/dt$  must complement  $iR$  Static and Dynamic Drop analysis ☠.*


Fast I transient

High average I
 
# Power Supply Impact on IC's Performances

*How the power is supplied to an integrated circuit may affects the performances of the system:*

- Power Supply noise limits the maximum operating frequency of an integrated circuit [PDN\_04, Free\_06, ...]*



**Freescall** gains 8% of performances by on chip bypassing

NB: C035 130nm  
C027 90nm

[Free\_06]

# Definitions

## ***Decoupling***

- ***The art and practice of breaking coupling between portions of systems and circuits to ensure proper operation.***


## ***Bypassing***

- ***The practice of adding a low-impedance path to shunt transient energy to ground at the source. Required for proper decoupling.***

[Cypress Semiconductor Corporation 1999]


# Bypassing Strategy, an Example: the Pentium 4™

## 4 levels of Bypassing

 


2. On PCB (Socket)

4. On Chip

 

1. On PCB (Source)

3. In Package

 


Too Expensive in a  
Wireless Terminal

# AGENDA


- 1- **Bandwidth of Interest**
- 2- Model of a Power Distribution System
- 3- Bypassing Examples
- 4- Bypassing Methods
- 5- IC and PCB Designers Point of View
- 6- Power Distribution System Model Extraction
- 7- Conclusion

# A Trapezoidal On-Chip Signal

$$t_r \ll T_{sig}$$

 


# Bandwidth of a Trapezoidal Signal

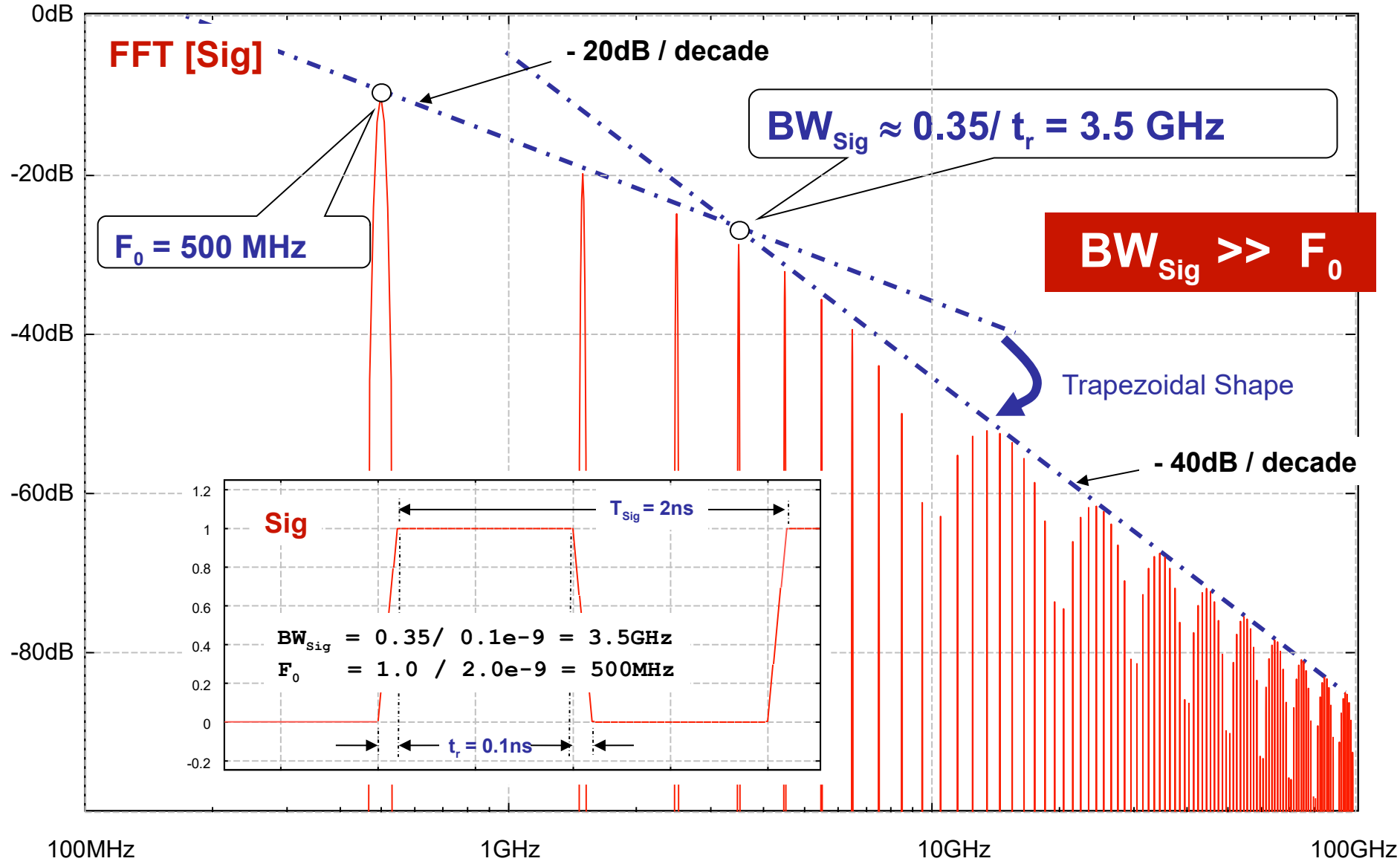



# Energy in a Trapezoidal Signal

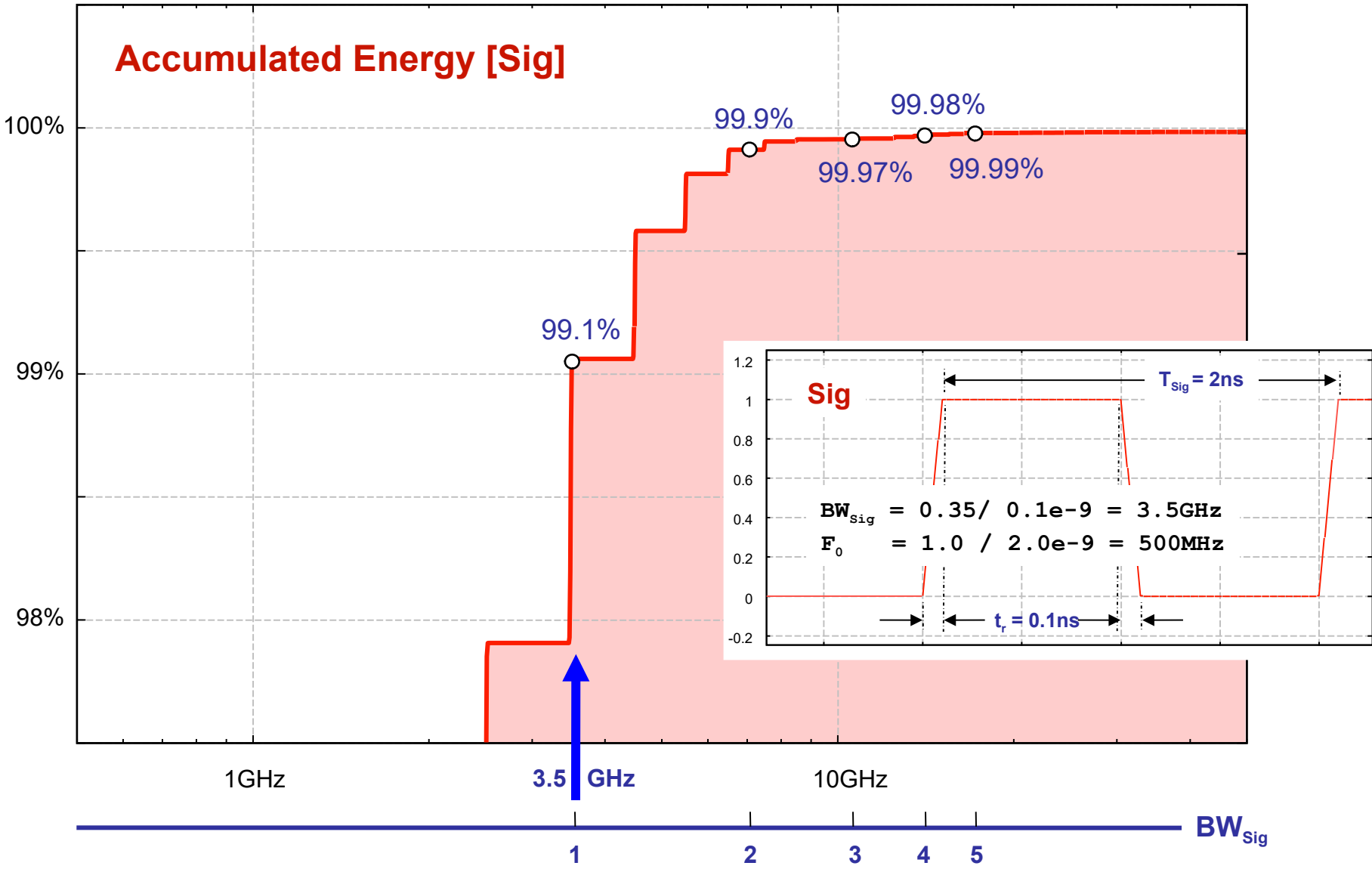


# AGENDA

- 1- Bandwidth of Interest
- 2- **Model of a Power Distribution System**
- 3- Bypassing Examples
- 4 Bypassing Methods
- 5- IC and PCB Designers Point of View
- 6- Power Distribution System Model Extraction
- 7- Conclusion

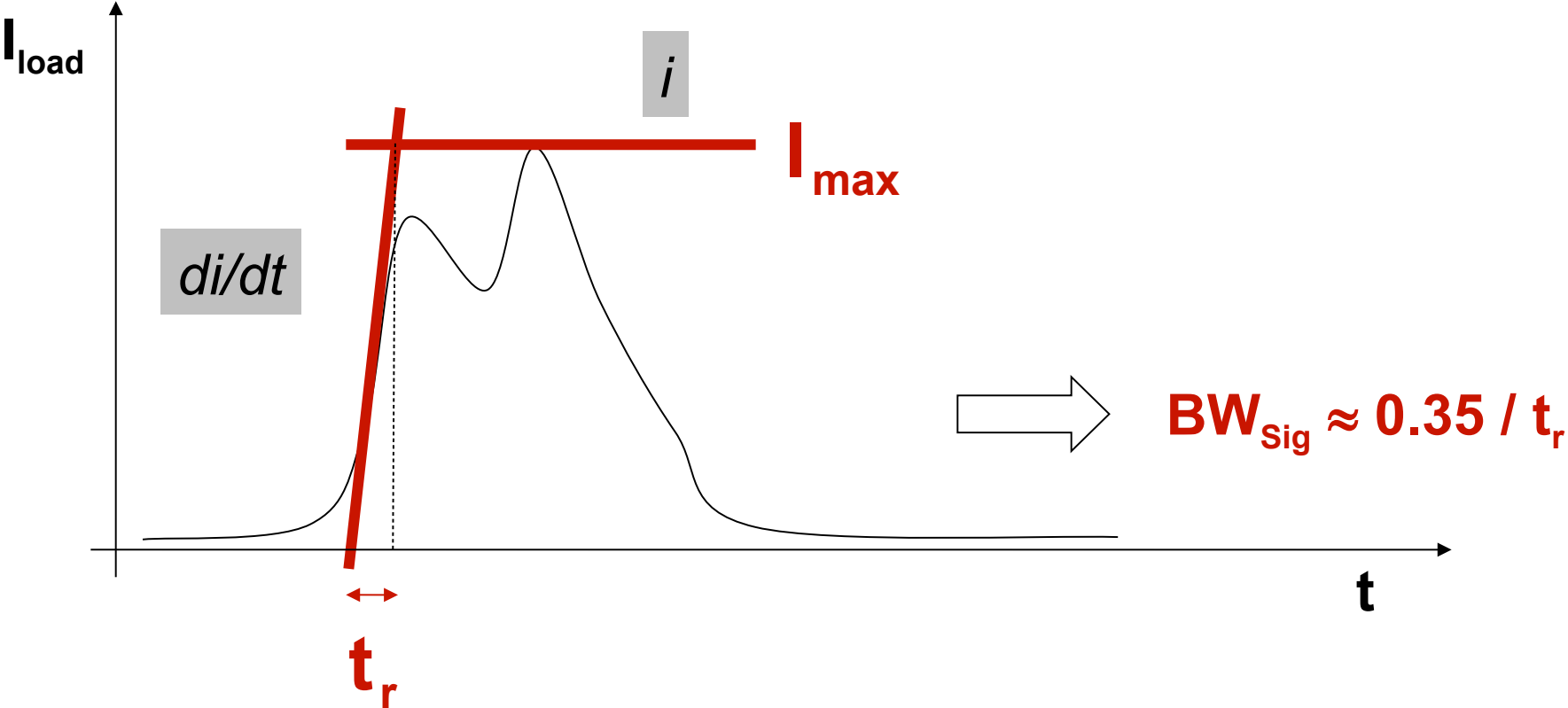
# Modeling with a Trapezoidal Simplified Model

In a **Power Distribution System**, the signal is a Current Surge.



# Simplified Model of a Power Distribution System: RLC

*NB: Global ground does not exist!*

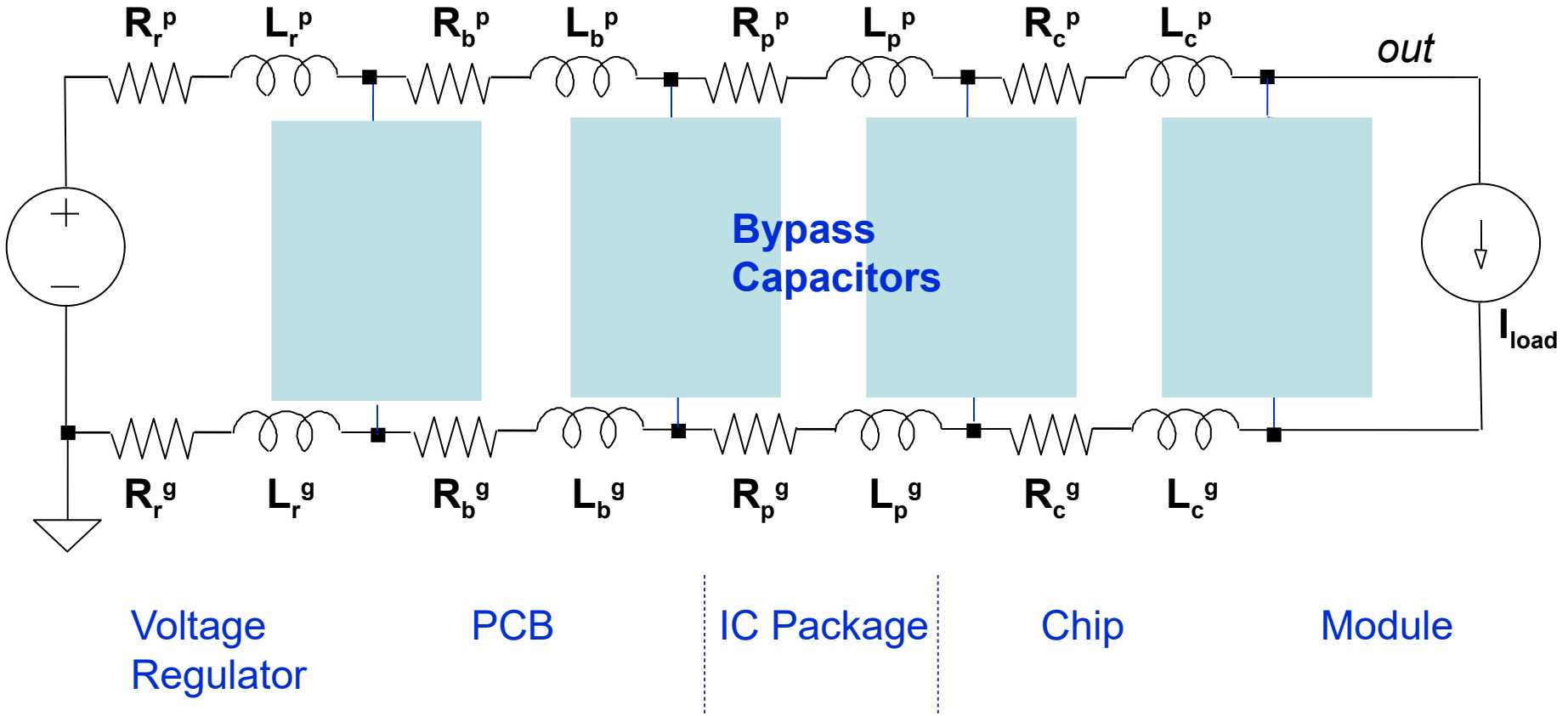

The power source and the load are connected through resistive and **inductive** parasitic impedances.

# Power Distribution System Target Impedance

$V_{dd}$  = Power Supply Voltage [V]

ToI = Allowed Ripple [%]

$I_{max}$  = Max Load Current [A]


$$R_{target} = V_{dd} \times (ToI / 100) / I_{max}$$

For example,

with an allowed ripple of 10% on a Vdd of 1V  
and a max load current of 100mA,  
the target impedance will be 1Ω


# Power Distribution System Target Impedance

$Z_{out}$  Magnitude,  $\log|\Omega|$

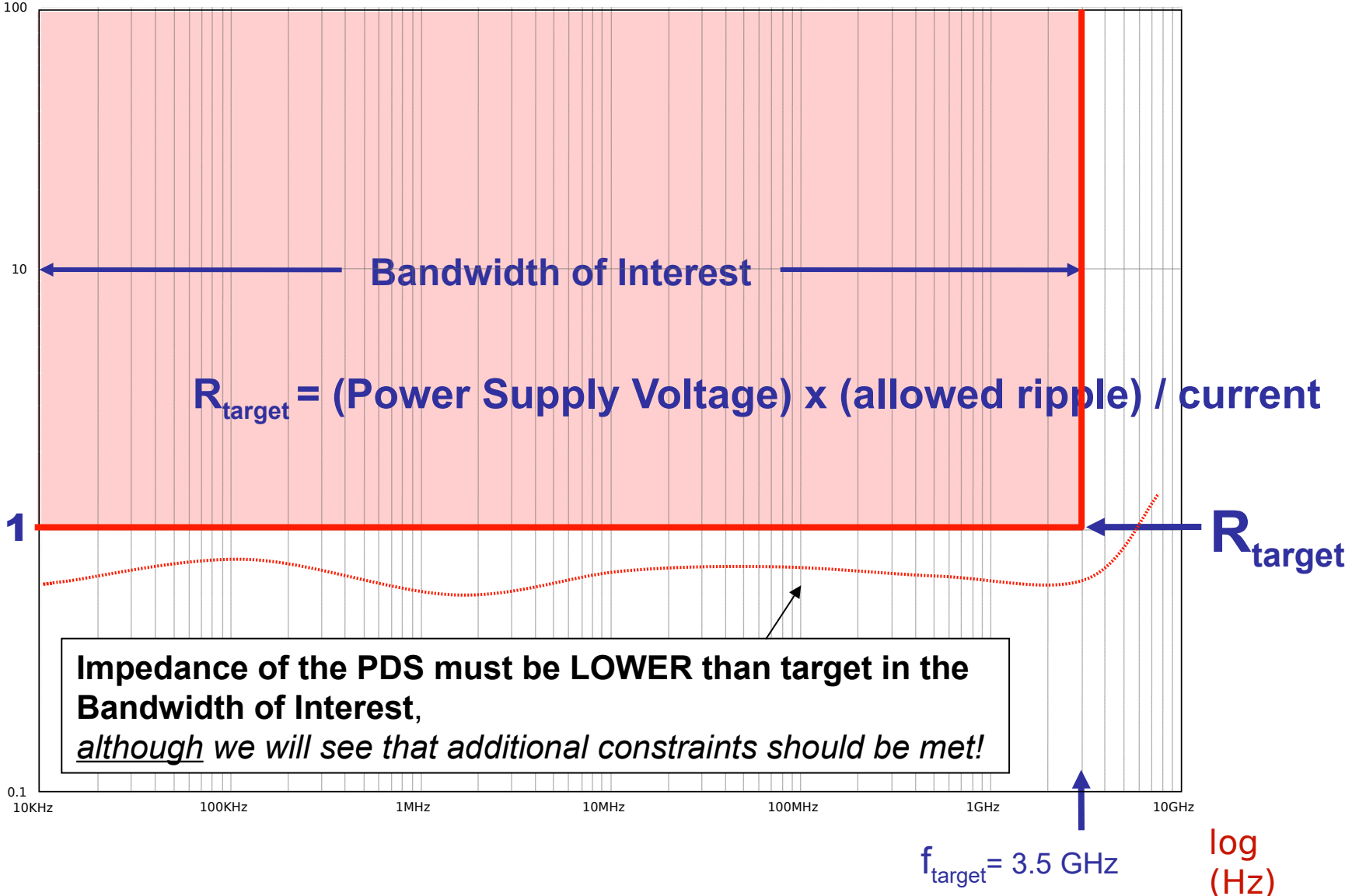

# PCB Bypassing does not Solve IC Issues

$Z_{out}$  Magnitude,  $\log|\Omega|$

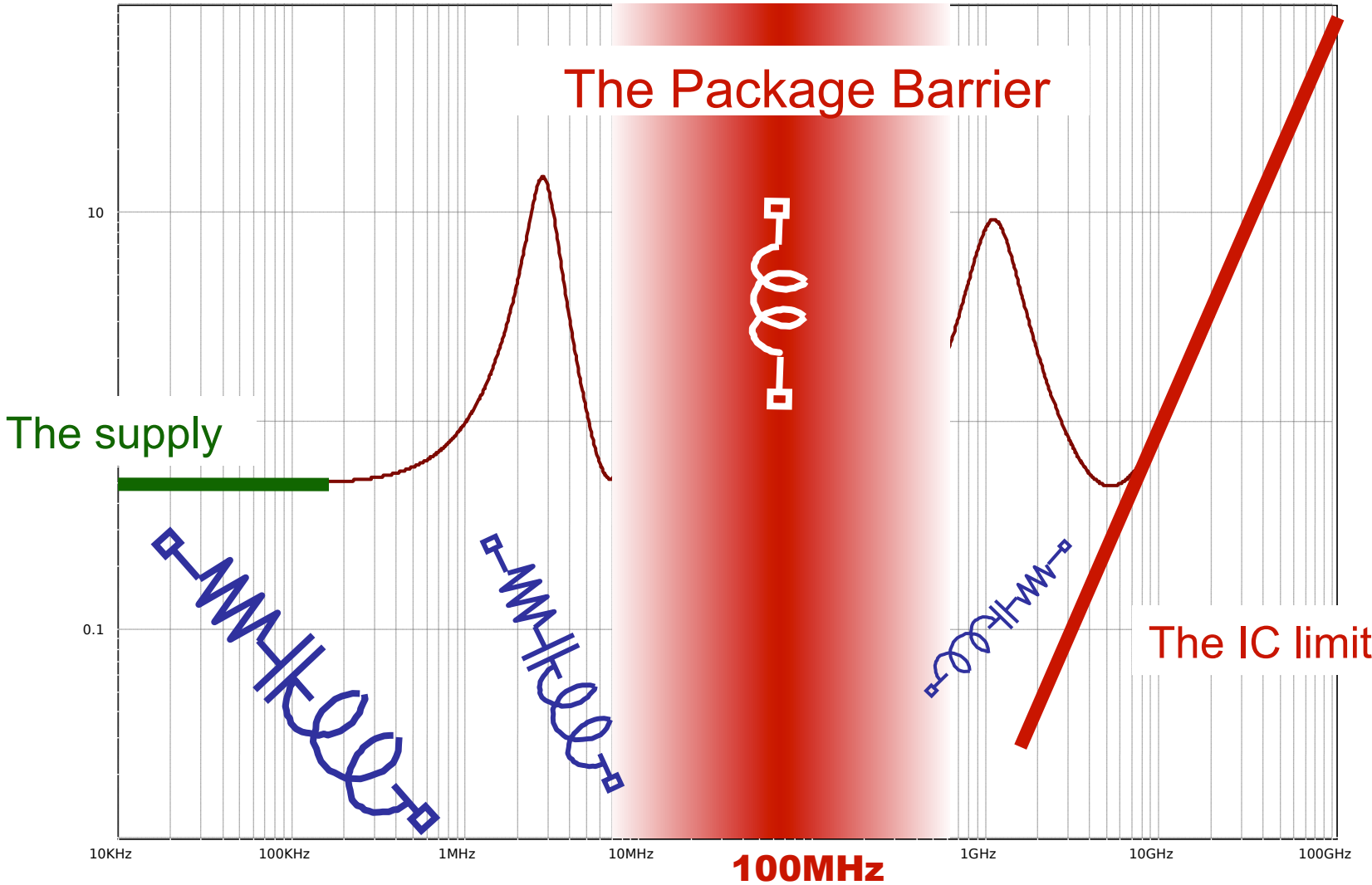

**100MHz**

log  
(Hz)

# AGENDA

- 1- Bandwidth of Interest
- 2- Model of a Power Distribution System
- 3- **Bypassing Examples**
- 4- Bypassing Methods
- 5- IC and PCB Designers Point of View
- 6- Power Distribution System Model Extraction
- 7- Conclusion



# FYI, Some Orders of Magnitude

Package 424ZQX

***0.3nH ... 5nH***

***15mΩ ... 180mΩ***

*0.1pF ... 0.6pF*

Bond Wire

***50mΩ /mm***

***1nH /mm***

*0.05pF /mm*

Typical PCB Line

***0.5nH /mm***

*0.1pF /mm*

*5mΩ /mm*

Via through 1.6mm PCB

***1.3nH***

0402 Capacitor

*100nF*

***0.5nH***


*25mΩ*

**Rule of Thumb**

**$L \approx 1\text{nH /mm}$**

# Linear Variation of L and R with the Circuit Dimensions

$$2\pi F_{res} = 1 / \sqrt{LC}$$

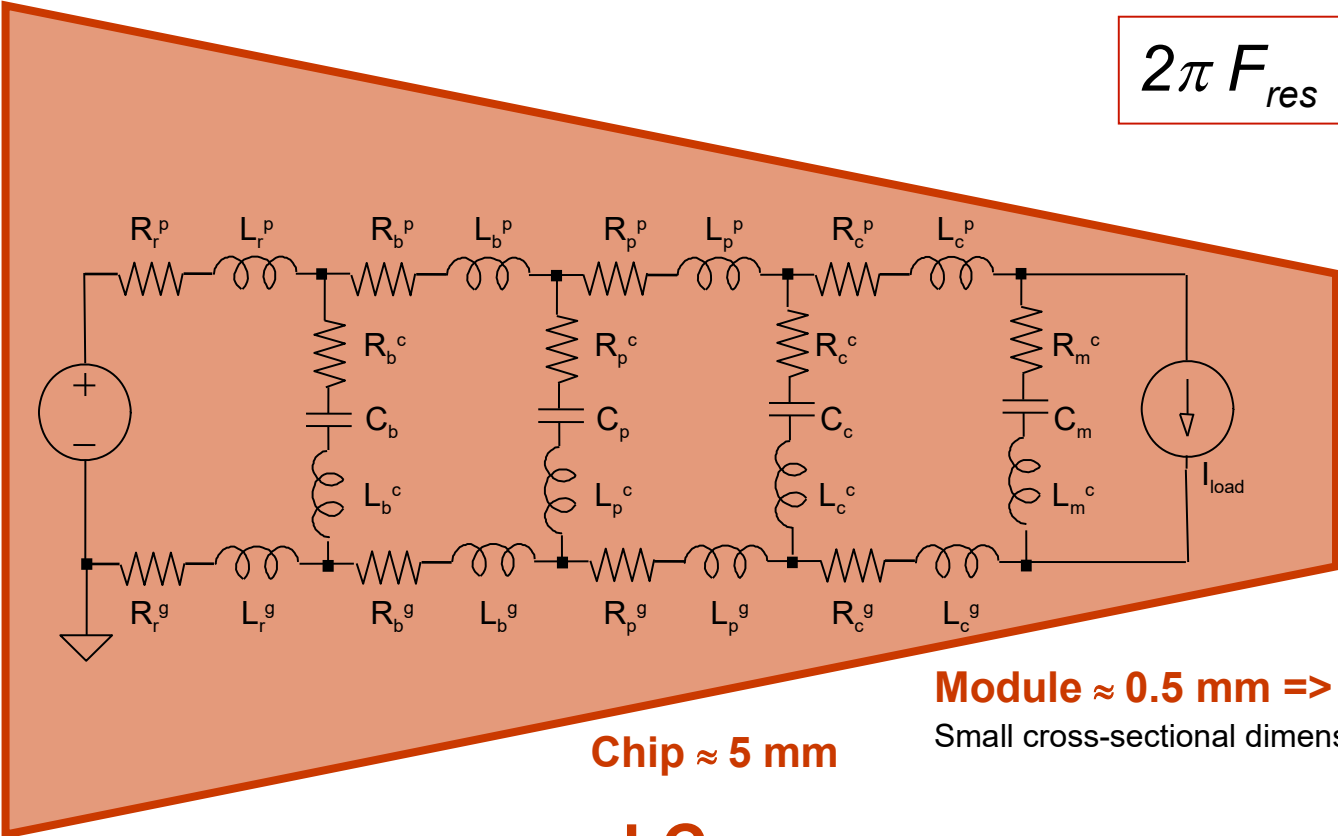

**Module  $\approx 0.5 \text{ mm} \Rightarrow R_{LC}$**

Small cross-sectional dimensions of the IC interconnect

**Chip  $\approx 5 \text{ mm}$**

**PCB  $\approx 50 \text{ mm} \Rightarrow R_{LC}$**

Large cross-sectional dimensions of PCB interconnect

*Physical dimensions*



$$\begin{aligned}
 L_r &\gg L_b \gg L_p \gg L_c \\
 R_r &\ll R_b \ll R_p \ll R_c \\
 C_b &\gg C_p \gg C_c \gg C_m
 \end{aligned}$$

# Our Example

\*\*\*\*\* TARGET

.PARMS Z0 1.00

\*\*\*\*\* PDN BOARD

.PARMS Rr 0.25

.PARMS Lr 50.0nH

.PARMS Rb 0.10

.PARMS Lb 10.00nH


\*\*\*\*\* PDN IC

.PARMS Rp 0.05

.PARMS Lp 1.00nH

.PARMS Rc 0.10

.PARMS Lc 0.10nH

 


VR


PCB

Package

IC

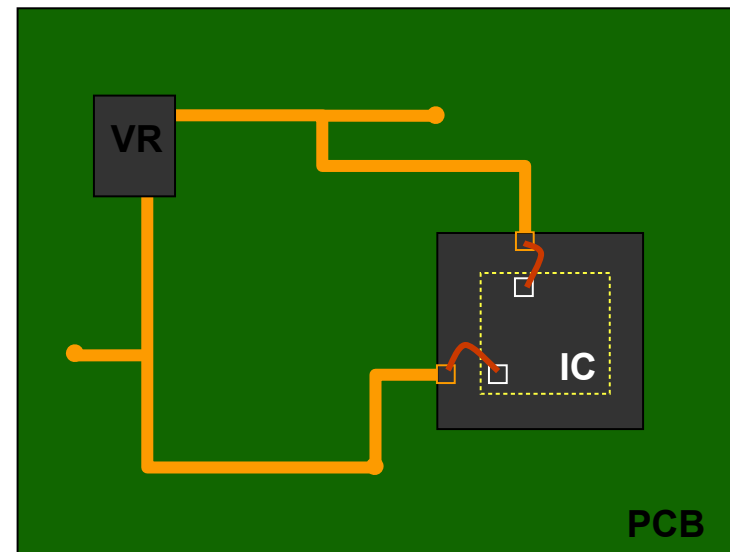

# PDS with No Bypass Capacitor

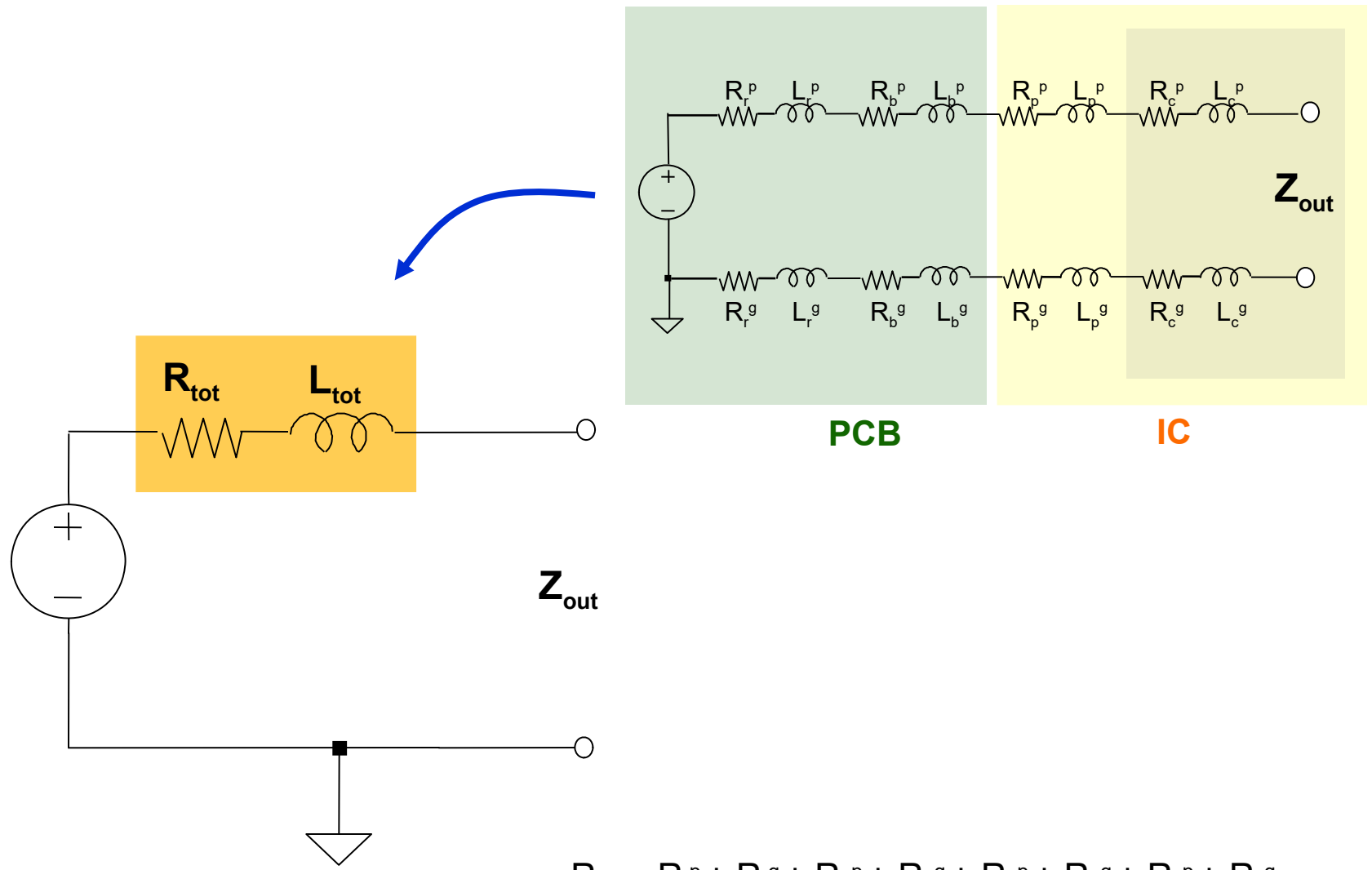


$$R_{tot} = R_r^p + R_r^g + R_b^p + R_b^g + R_p^p + R_p^g + R_c^p + R_c^g$$


$$L_{tot} = L_r^p + L_r^g + L_b^p + L_b^g + L_p^p + L_p^g + L_c^p + L_c^g$$

# Impedance of a PDS with **No** Bypass Capacitor


$Z_{out}$  Magnitude,  $\log|\Omega|$

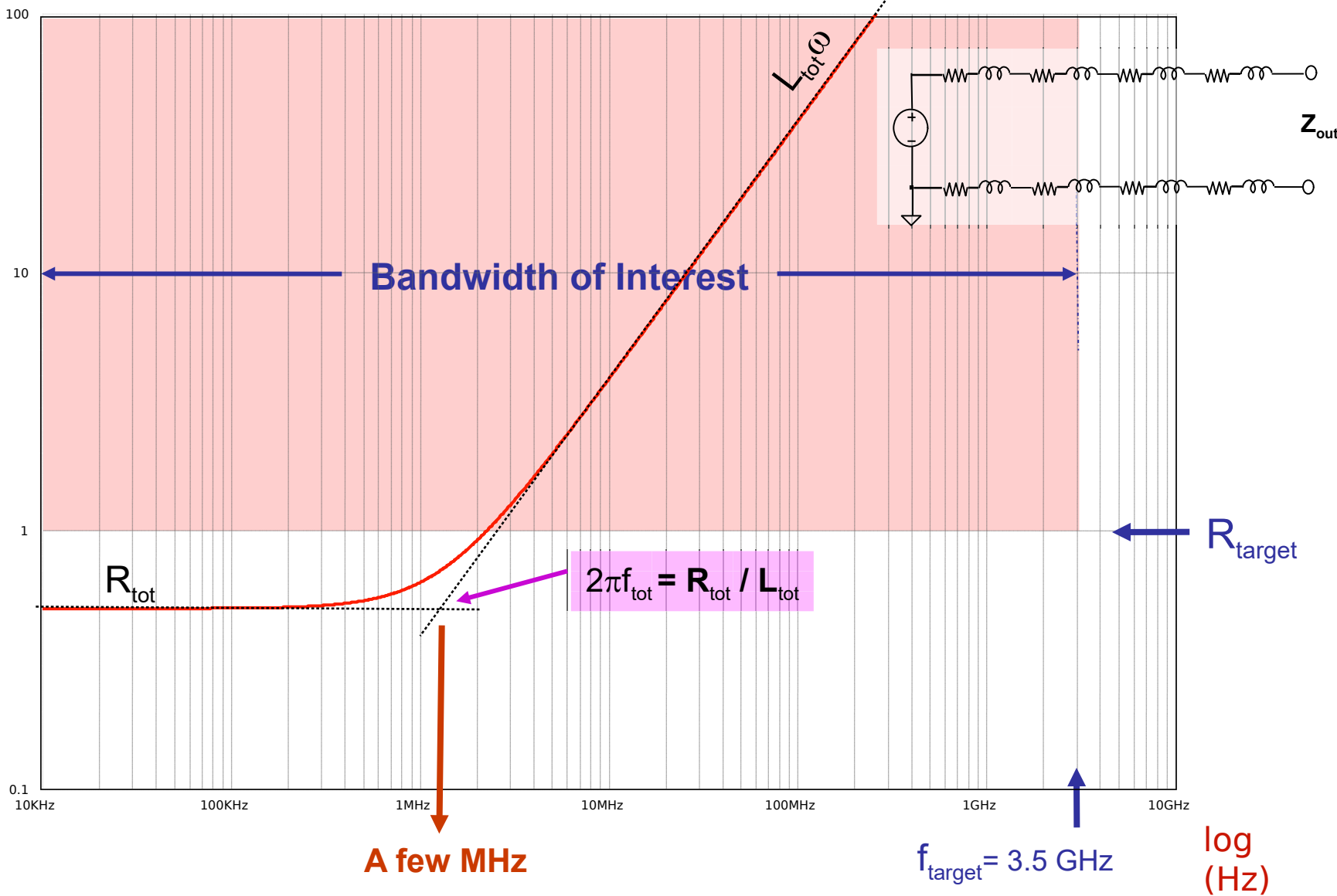

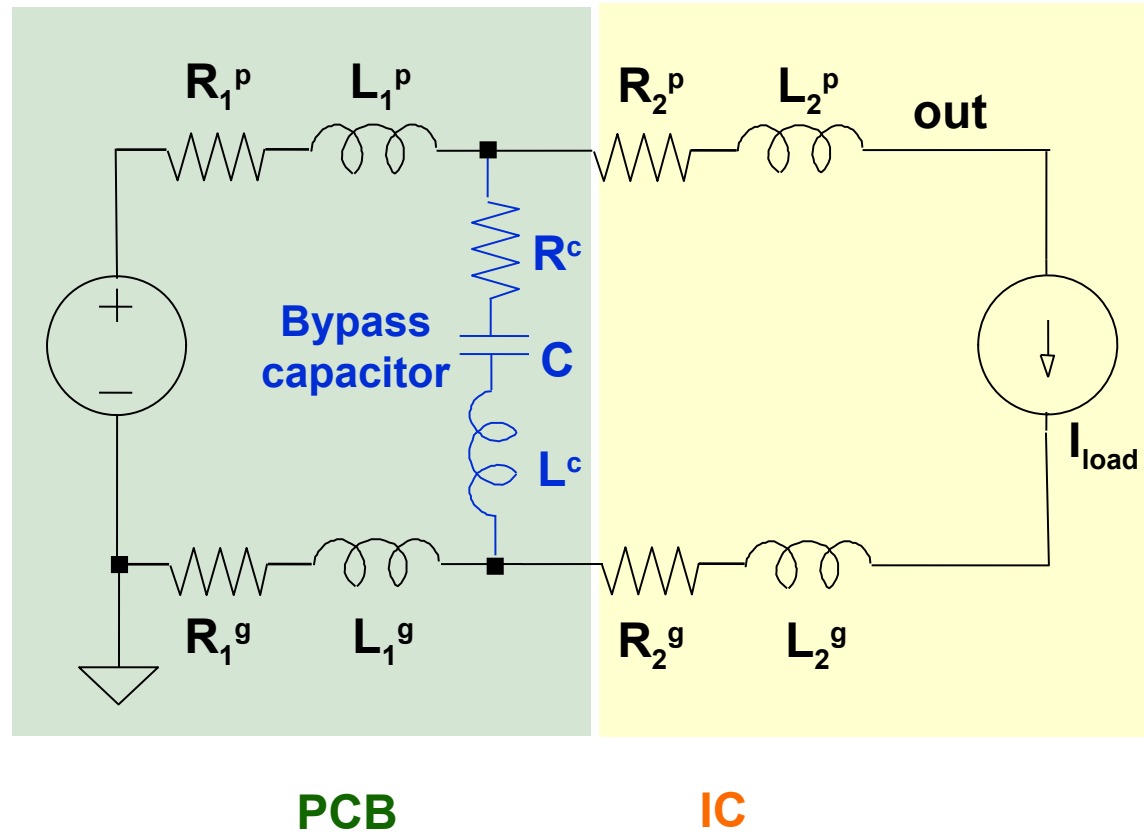
# PDS with a Single Bypass Capacitor on PCB



# PDS with a Single Bypass Capacitor

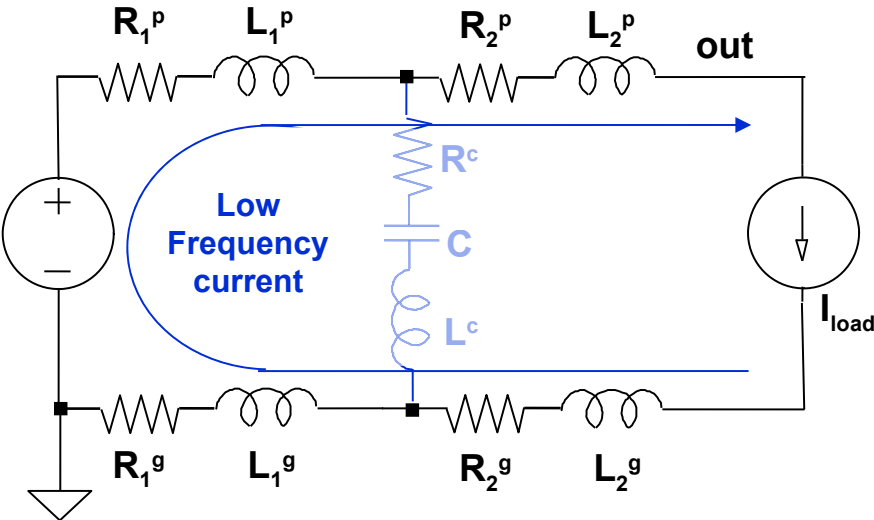

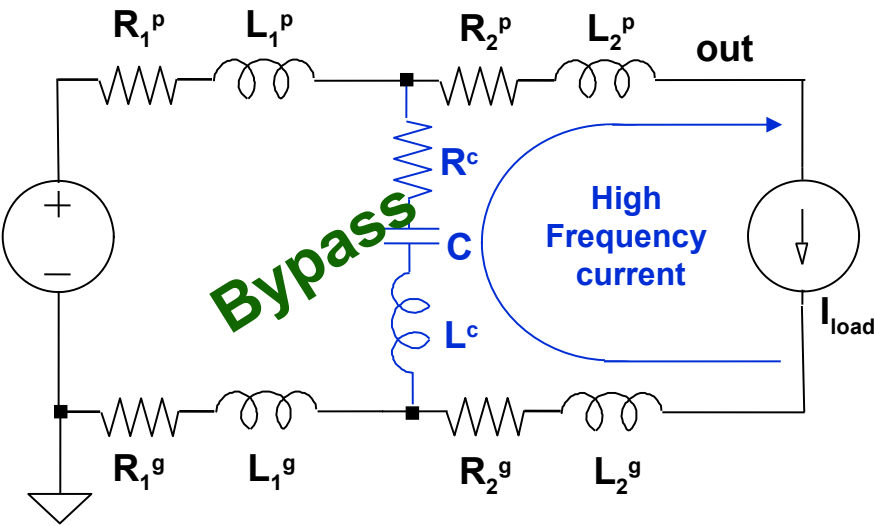Below  $f_{res}$ , the bypass capacitance is relatively high.




Assuming  $L^c < L_1$ ,

Above  $f_{res}$ , the bypass capacitance is lower than the (R1, L1) path.


# Impedance of a PDS with a Single Bypass Capacitor

$Z_{out}$  Magnitude,  $\log|\Omega|$

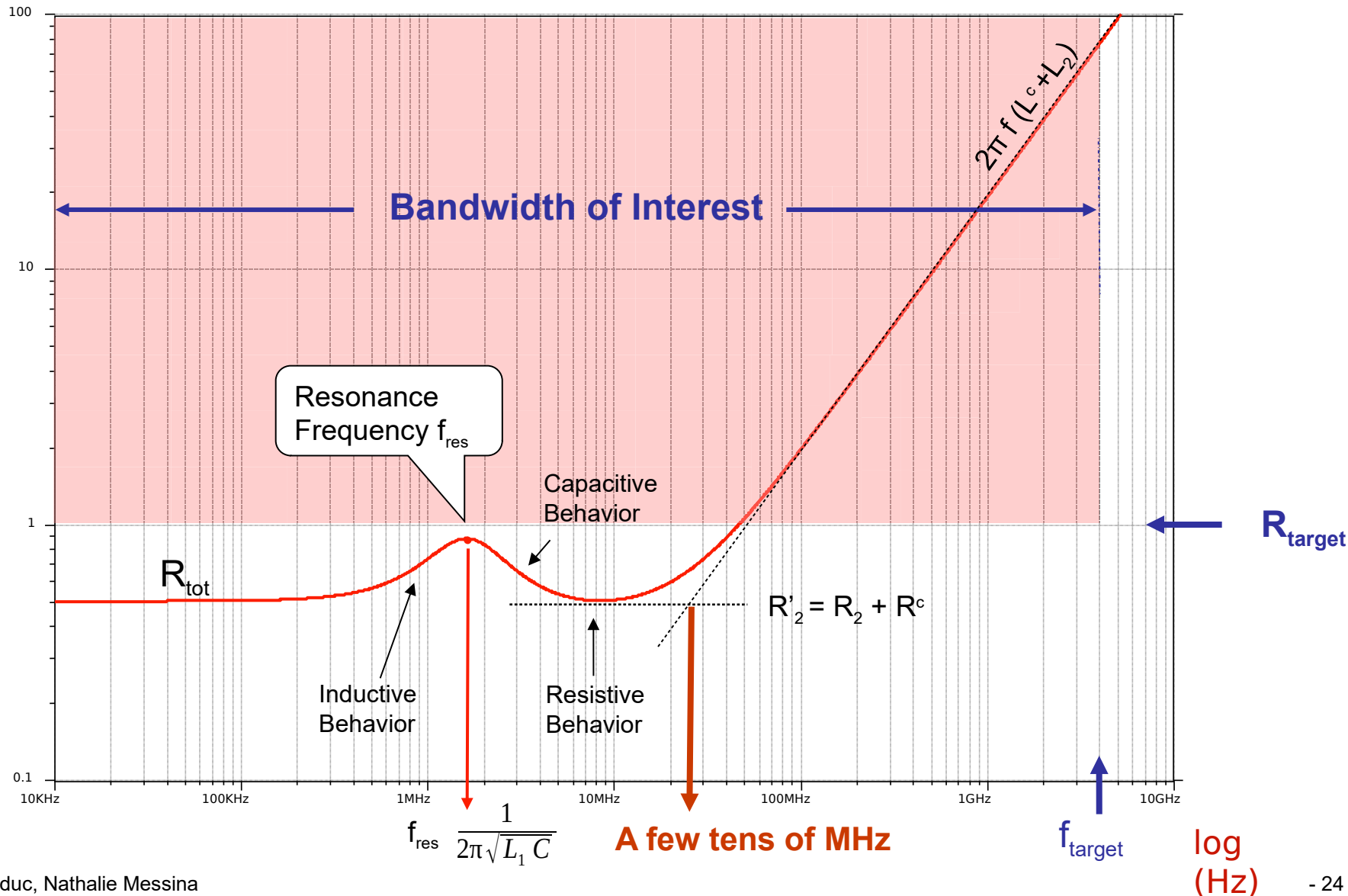



 
# Transient of a PDS with a **Single** Bypass Capacitor


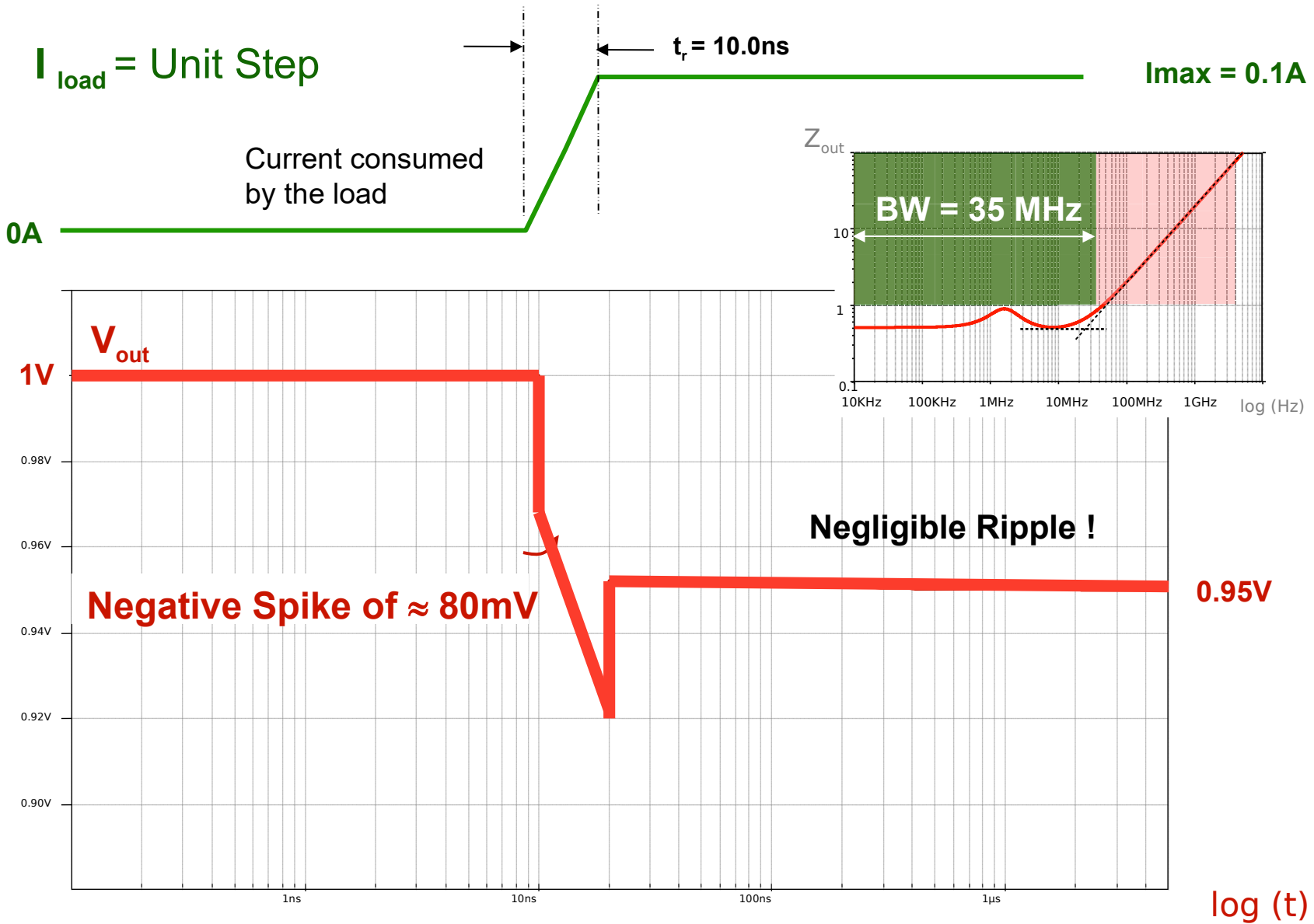
# Just Curious: Let's Increase $t_r$ to 10ns



# Limitation from a Single Bypass Capacitor

- The device should have a high capacity to **store and release** a sufficient **amount** of energy


$$C > L_1 / Z_{\text{target}} (R_1 + R^c)$$

- To supply sufficient power at high frequencies, the device should be able to **store and release** energy at a sufficient **delivery rate**.

$$(L_2 + L^c) < Z_{\text{target}} / 2\pi f_{\text{target}}$$

**The condition of low inductance path cannot be satisfied.  
Inductance  $L_2$  is the issue:**

 
$$\begin{aligned} L_2 &\approx 1 \text{ nH} \\ f_{\text{target}} &\approx 3 \text{ GHz} \\ Z_{\text{target}} &\approx 1 \Omega \\ (1\text{e-}9 + L^c) &\gg 1 / (6.28 \times 3\text{e}9) \end{aligned}$$


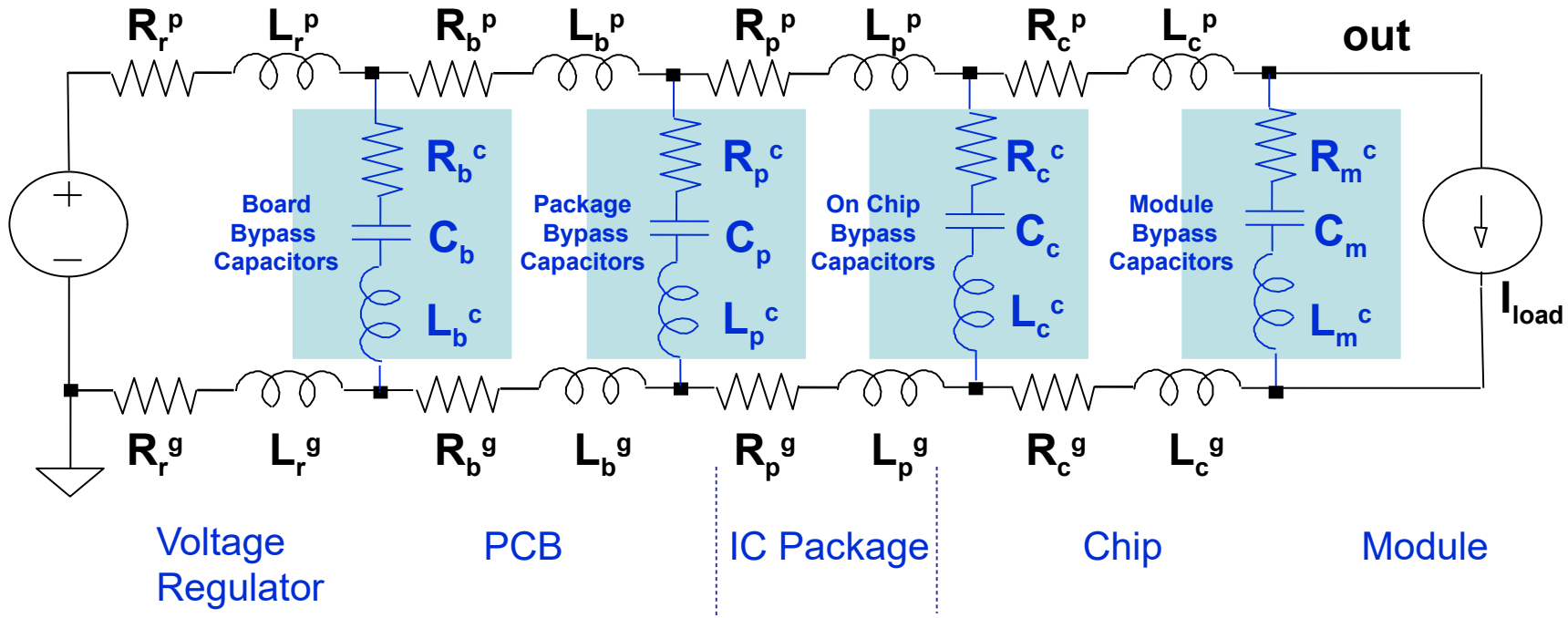
# Hierarchical Placement of Bypass Capacitors


Exploits the tradeoff between the capacitance and the parasitic series inductance of a bypass capacitor.

The bypass capacitor at each stage is effective within a limited frequency range. The ranges of effectiveness overlap each other, reaching  $f_{\text{target}}$ .




# Impedance of a PDS with Hierarchical Bypass Capacitors

$Z_{out}$  Magnitude,  $\log|\Omega|$

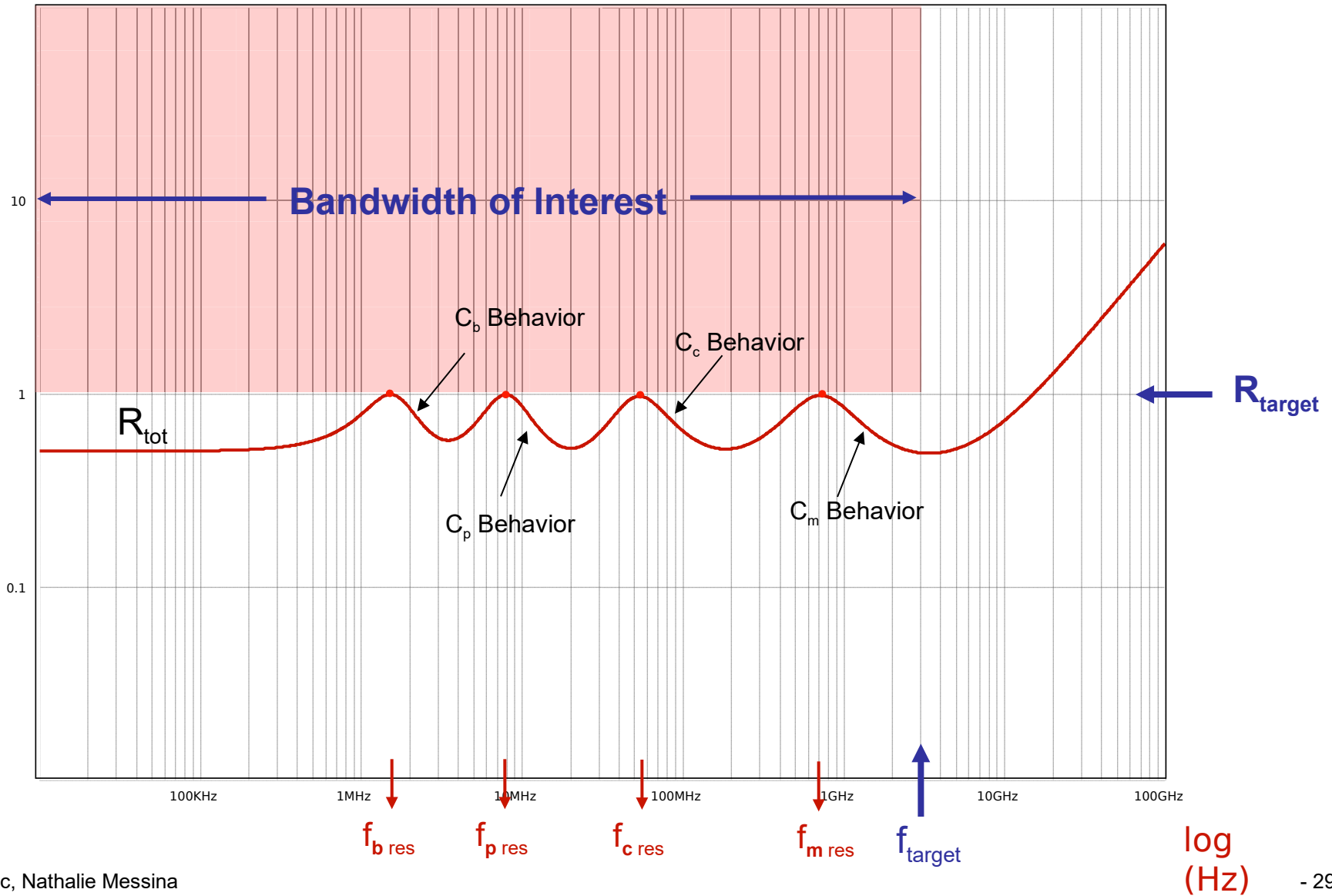

 
# Transient of a PDS with Hierarchical Bypass Capacitors



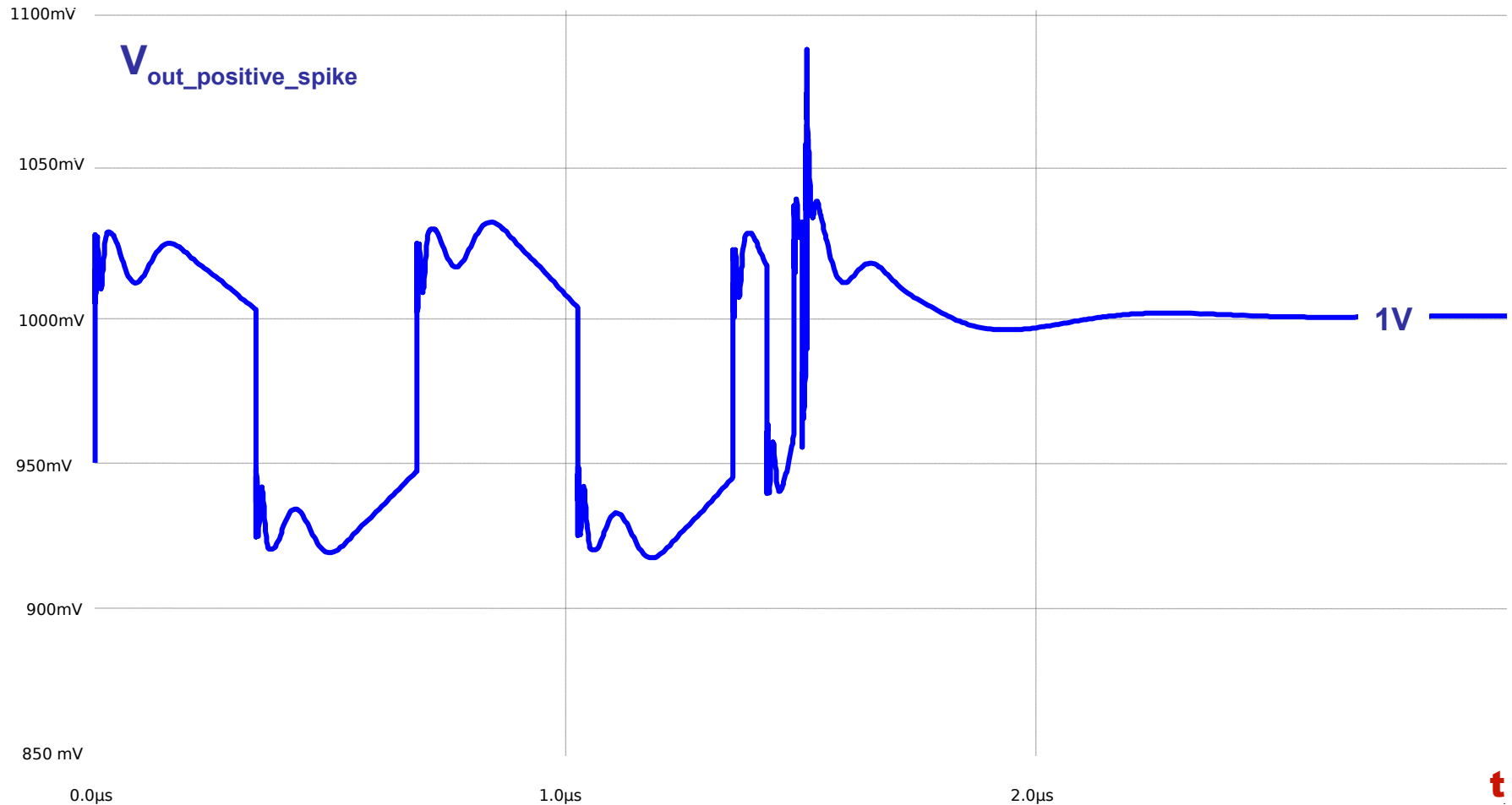
# Worst Case Peak Transient

To get the worse case of spikes on the supply voltage, we apply an “appropriate” stimulus as  $I_{load}$ .


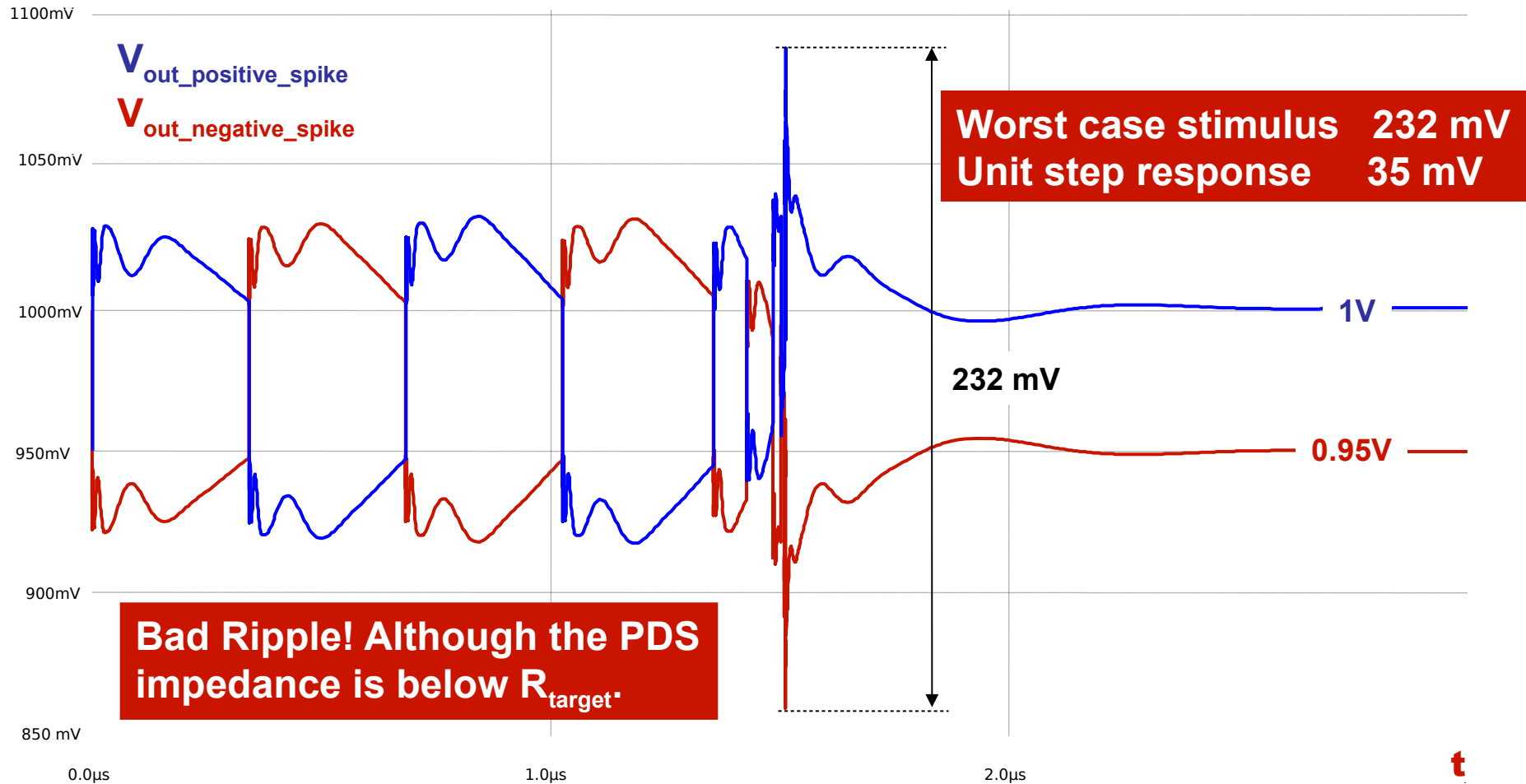
# Worst Case Peak-to-Peak Transient

We apply the negative and positive stimulus to get the peak to peak value.







# Flat Impedance of a PDS with Hierarchical Bypass Caps

$Z_{out}$  Magnitude,  $\log|\Omega|$

 It is possible to flatten the PDS impedance by proper tuning of the bypass capacitors. Method called full impedance compensation will be explained later.


 
# Transient of a PDS with a Flat Impedance




# AGENDA


- 1- Bandwidth of Interest
- 2- Model of a Power Distribution System
- 3- Bypassing Examples
- 4- **Bypassing Methods**
- 5- IC and PCB Designers Point of View
- 6- Power Distribution System Model Extraction
- 7- Conclusion
 
# Method to Flatten the Impedance of a PDS with HBC

A full impedance compensation at each bypassing stage




$Z_{out}$  Magnitude,  $\log|\Omega|$

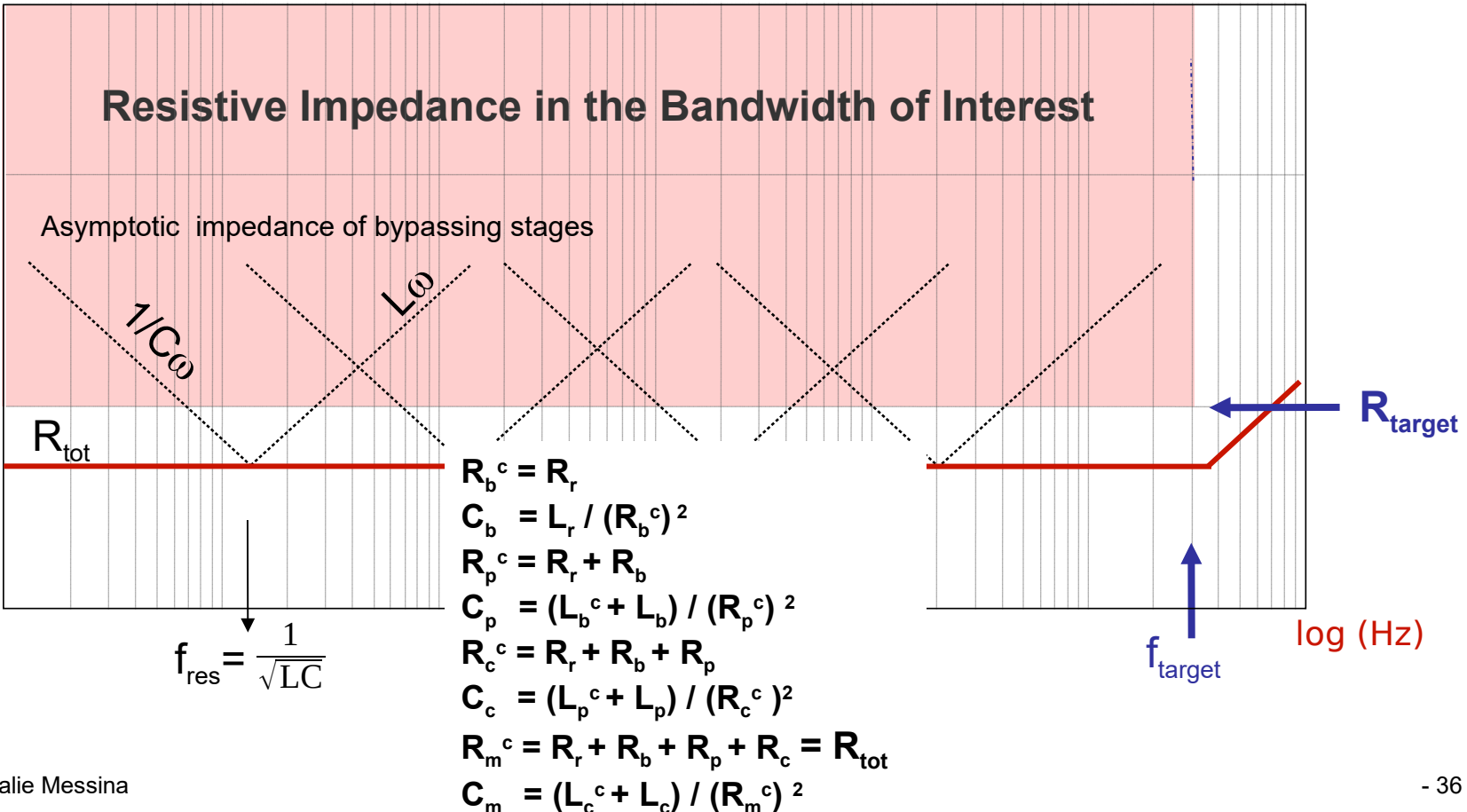
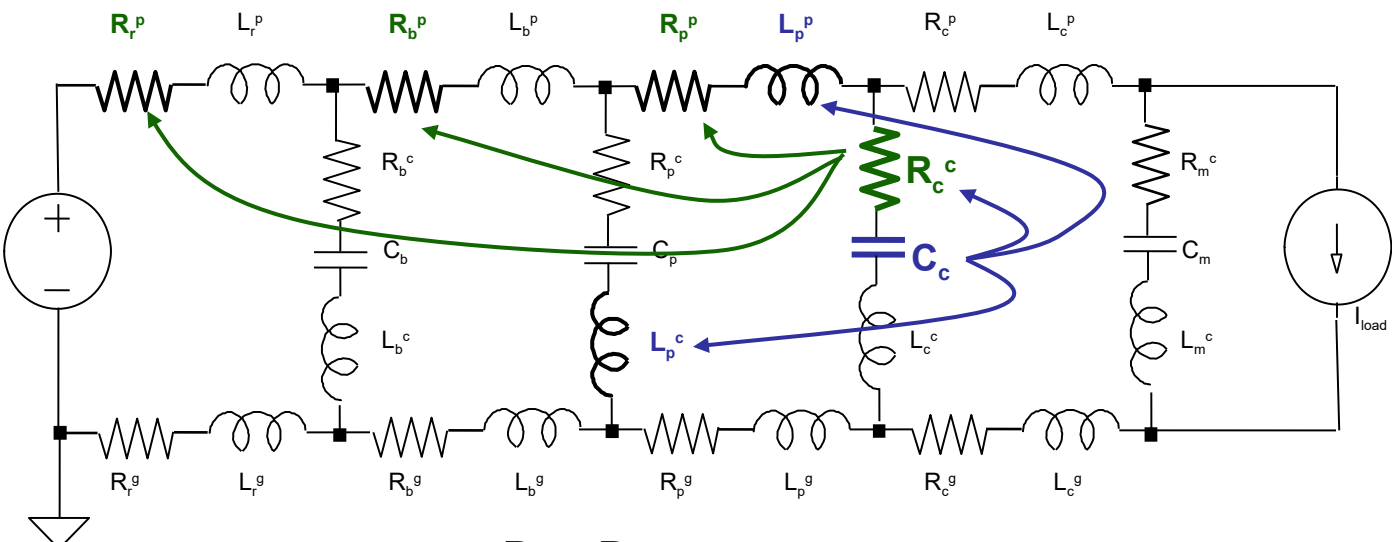
# Method to Flatten the Impedance of a PDS with HBC

A full impedance compensation at each bypassing stage



$$R_b^c = R_r$$

$$C_b = L_r / (R_b^c)^2$$

$$R_p^c = R_r + R_b$$

$$C_p = (L_b^c + L_b) / (R_p^c)^2$$



$$R_c^c = R_r + R_b + R_p$$

$$C_c = (L_p^c + L_p) / (R_c^c)^2$$


$$R_m^c = R_r + R_b + R_p + R_c = R_{tot}$$

$$C_m = (L_c^c + L_c) / (R_m^c)^2$$

# How it Works?

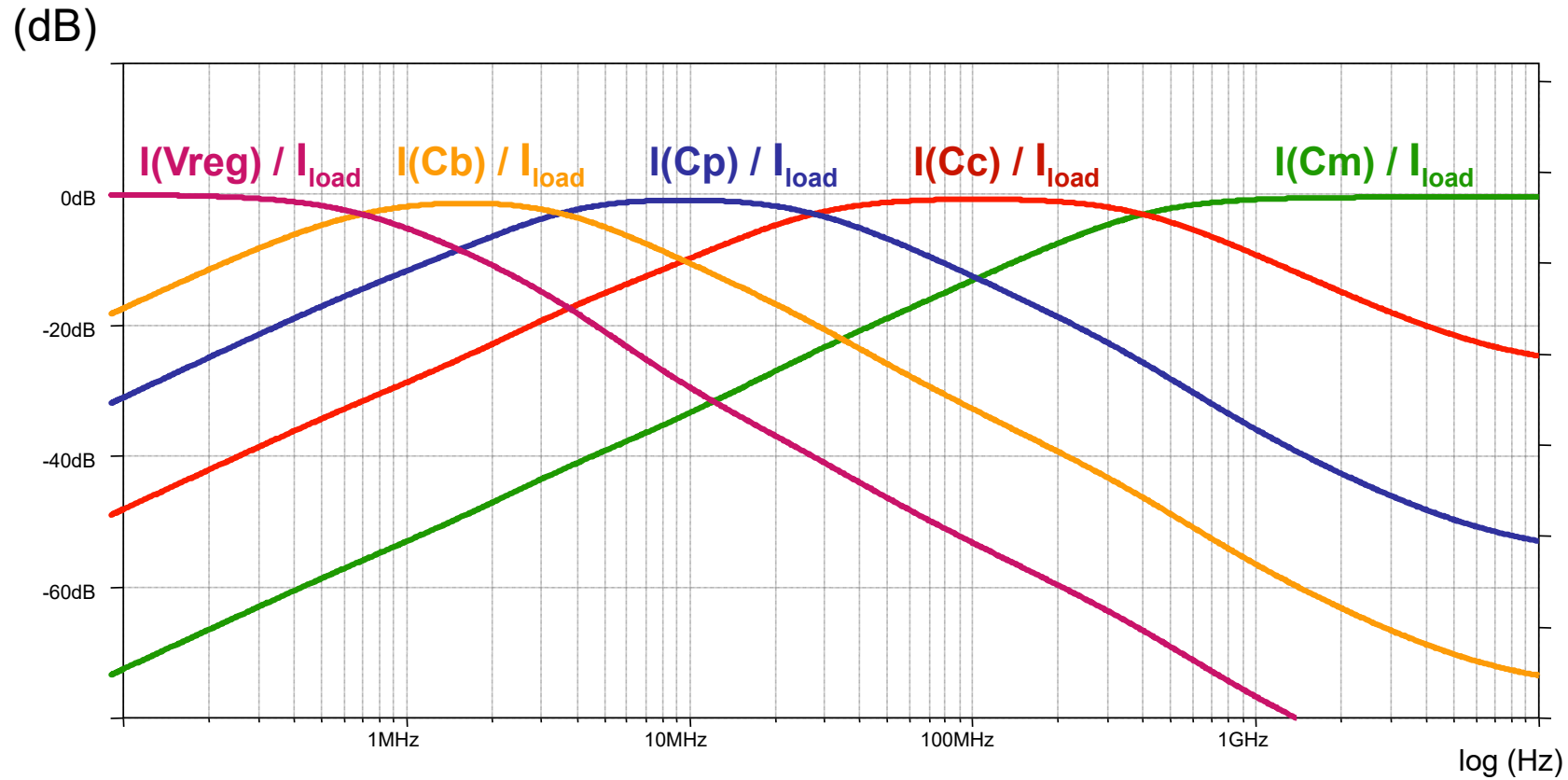 

# Bypass Capacitors Computation

 

\*\*\*\*\* TARGET

.PARMS Z0 1.00

\*\*\*\*\* PDN BOARD

```
.PARMS Rr 0.25
.PARMS Lr 50.0nH

.PARMS Rb 0.10
.PARMS Lb 10.00nH
```

\*\*\*\*\* BYPASS ON THE BOARD

```
.PARMS RCb 0.25
.PARMS Cb 800.00nF
.PARMS LCb 5.00nH

.PARMS RCp 0.35
.PARMS Cp 122.4nF
.PARMS LCp 1.50nH
```

$$R_b^c = R_r$$

$$C_b = L_r / (R_b^c)^2$$

$$R_p^c = R_r + R_b$$

$$C_p = (L_b^c + L_b) / (R_p^c)^2$$

\*\*\*\*\* PDN IC

```
.PARMS Rp 0.05
.PARMS Lp 1.00nH

.PARMS Rc 0.10
.PARMS Lc 0.10nH
```

\*\*\*\*\* BYPASS ON THE IC

```
.PARMS RCc 0.4
.PARMS Cc 15.6nF
.PARMS LCc 0.10nH

.PARMS RCm 0.5
.PARMS Cm 0.75nF
.PARMS LCm 0.01nH
```

$$R_c^c = R_r + R_b + R_p$$


$$C_c = (L_p^c + L_p) / (R_c^c)^2$$

$$R_m^c = R_r + R_b + R_p + R_c = R_{tot}$$

$$C_m = (L_c^c + L_c) / (R_m^c)^2$$


# Flat Impedance of a PDS with Hierarchical Bypass Caps

$Z_{out}$  Magnitude,  $\log|\Omega|$

 



# The ESR Issue

 

\*\*\*\*\* TARGET

.PARMS Z0 1.00

\*\*\*\*\* PDN BOARD

.PARMS Rr 0.25  
 .PARMS Lr 50.0nH  
 .PARMS Rb 0.10  
 .PARMS Lb 10.00nH

\*\*\*\*\* BYPASS ON THE BOARD


.PARMS RCb 0.25  
 .PARMS Cb 800.00nF  
 .PARMS LCb 5.00nH  
 .PARMS RCp 0.35  
 .PARMS Cp 122.4nF  
 .PARMS LCp 1.50nH

\*\*\*\*\* PDN IC

.PARMS Rp 0.05  
 .PARMS Lp 1.00nH  
 .PARMS Rc 0.10  
 .PARMS Lc 0.10nH

\*\*\*\*\* BYPASS ON THE IC

 
.PARMS RCc 0.4  
 .PARMS Cc 15.6nF  
 .PARMS LCc 0.10nH  
 .PARMS RCm 0.5  
 .PARMS Cm 0.75nF  
 .PARMS LCm 0.01nH




Impossible to realize such large ESR on Chip

# Big V Impedance of a PDS

$Z_{out}$  Magnitude,  $\log|\Omega|$

 

# The Big V Values

 

## Values for a Flat Impedance

\*\*\*\*\* BYPASS ON THE BOARD

```
.PARMS RCb 0.25
.PARMS Cb 800.00nF
.PARMS LCb 5.00nH

.PARMS RCp 0.35
.PARMS Cp 122.4nF
.PARMS LCp 1.50nH
```

## Values for a BigV Impedance

\*\*\*\*\* BYPASS ON THE BOARD

```
.PARMS RCb 0.25
.PARMS Cb 800.00nF
.PARMS LCb 5.00nH

.PARMS RCp 0.35
.PARMS Cp 122.4nF
.PARMS LCp 1.50nH
```

\*\*\*\*\* BYPASS ON THE IC



```
.PARMS RCc 0.4
.PARMS Cc 15.6nF
.PARMS LCc 0.10nH

.PARMS RCm 0.5
.PARMS Cm 0.75nF
.PARMS LCm 0.01nH
```


\*\*\*\*\* BYPASS ON THE IC

```
.PARMS RCc 0.01
.PARMS Cc 4.0nF
.PARMS LCc 0.10nH

  
.PARMS RCm 0.01
.PARMS Cm 35.0nF
.PARMS LCm 0.01nH
```


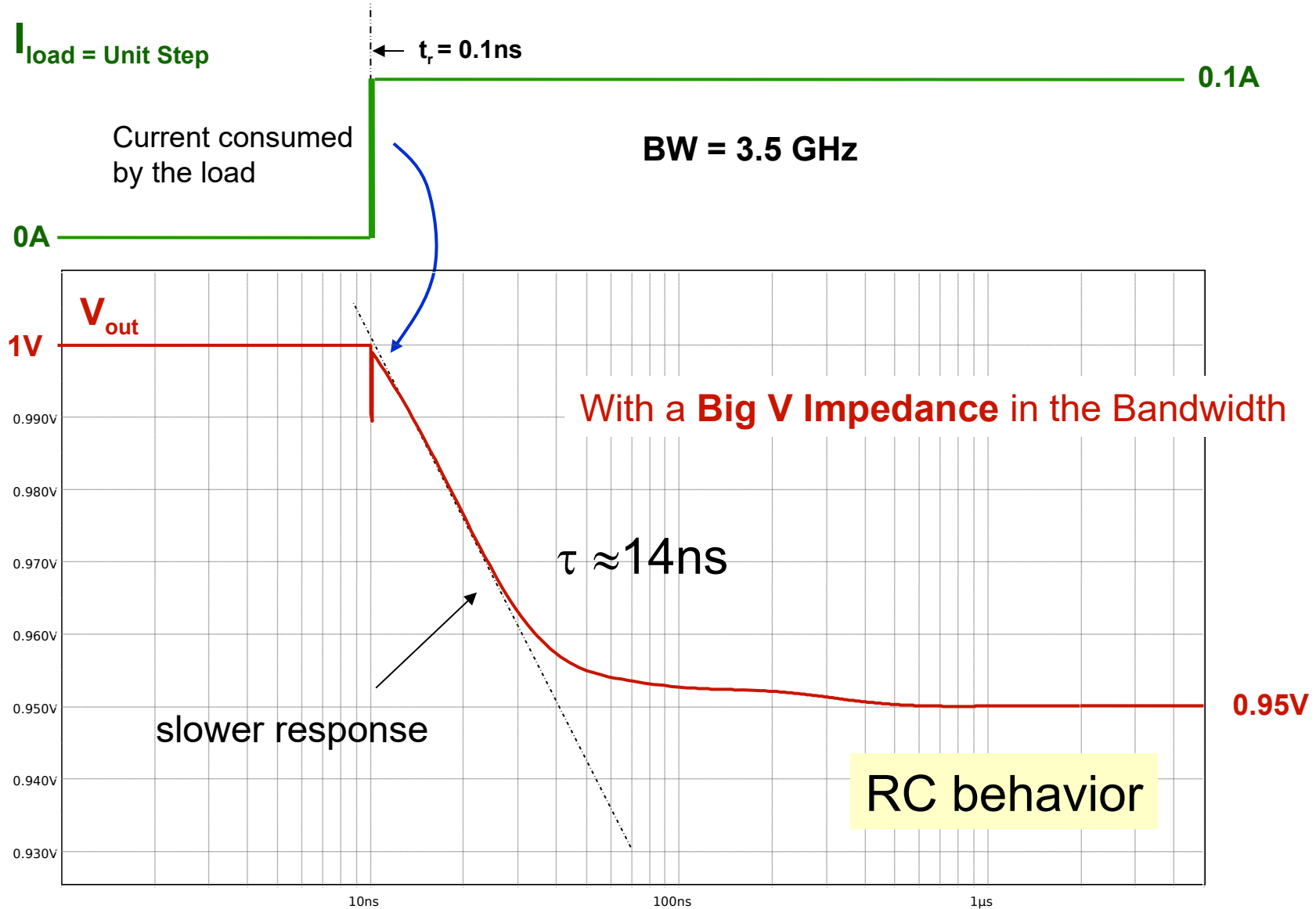
# Transient on a PDS with Big V Impedance


 
# Transient on a PDS around the Impedance Dip




Load Current @ 275 MHz



**Full Impedance Compensation**

 **Load**


If the operating frequency coincides to the frequency dip



**Package**

**Big V**

Big V is better!

 


**Load**

# AGENDA


- 1- Bandwidth of Interest
- 2- Model of a Power Distribution System
- 3- Bypassing Examples
- 4- Bypassing Methods
- 5- **IC and PCB Designers Point of View**
- 6- Power Distribution System Model Extraction
- 7- Conclusion

# PCB Design, IC Design: Impedance Matching

$$R_{tot} = R_{Ext} + R_{IC}$$

 

 
PCB bypassing,  
 $func(F_{match}, R_{IC}, R_{Ext})$




$R_{Ext} \rightarrow$

$F_{match}$

$\leftarrow R_{IC}$

 



=

 

Full power  
 distribution  
 system  
 bypassing

IC bypassing,  
 $func(F_{match}, R_{IC}, R_{Ext})$

# The IC Designer Point of View

  

According to the design methodology presented in the previous slides,


the IC designer needs to fix the appropriate **Resistance Budget**  $R_{Ext}$  of the external power supply to obtain the specified performances.

The designer will use the **BigV method** to choose the bypass capacitors on the IC.

The IC designer will communicate to the PCB designer the resistance budget  $R_{Ext}$ , the internal resistance of the IC  $R_{IC}$  and the frequency  $F_{match}$ .




# The Job of the IC Designer

 

PCB


The IC must behave as a resistance  $R_{IC}$  at  $F_{match}$

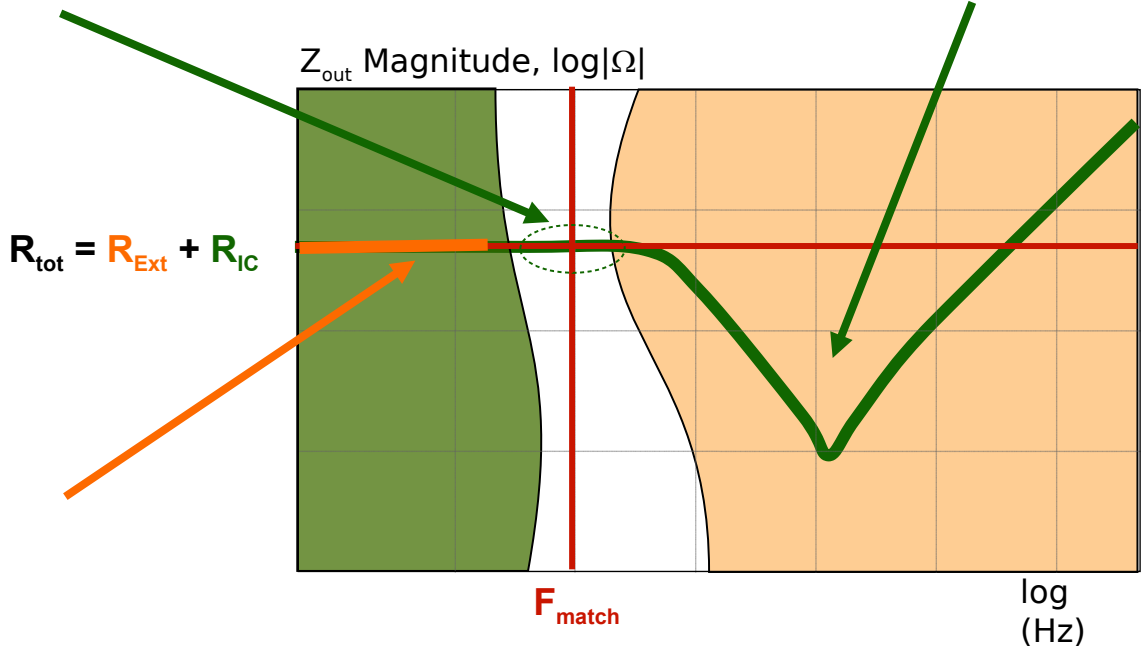**BigV** bypassing method is recommended for frequencies above  $F_{match}$



The PCB is modeled as a resistance  $R_{Ext}$

# The PCB Designer Point of View

 

According to the design methodology presented in the previous slides,


the PCB designer needs to know the **Resistance Budget**  $R_{Ext}$  of the power supply, the **Resistance of the IC**  $R_{IC}$  and the **Frequency**  $F_{match}$  to realize the impedance matching.

These resistances are provided by the IC vendor.  $R_{Ext}$  includes the PCB line resistance and the internal resistance of the voltage regulator.

$$R_{Ext} = R_{Regulator} + R_{PCB\ line}$$

The PCB designer will then use the **Full Impedance Compensation method** to choose the bypass capacitors on the PCB.


# The PCB Designer Point of View

 

The PCB must behave as a resistance  $R_{ext}$  below  $F_{match}$

The IC is modeled as a resistance  $R_{IC}$

$$R_{tot} = R_{Ext} + R_{IC}$$

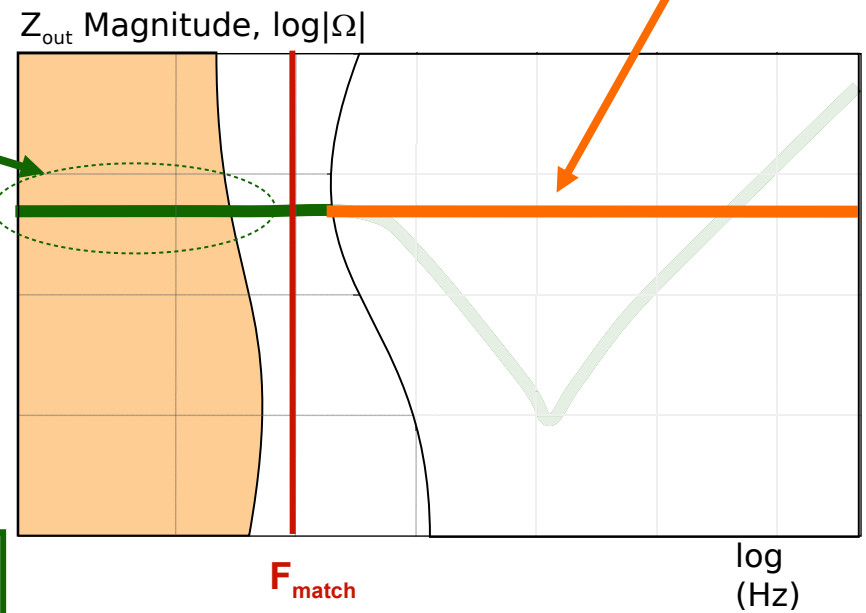


Using the  $R_{Ext}$ ,  $R_{IC}$  and the Frequency  $F_{match}$ , the PCB designer is able to get a perfect impedance matching.


# AGENDA

- 1- Bandwidth of Interest
- 2- Model of a Power Distribution System
- 3- Bypassing Examples
- 4- Bypassing Methods
- 5- IC and PCB Designers Point of View
- 6- **Power Distribution System Model Extraction**
- 7- Conclusion
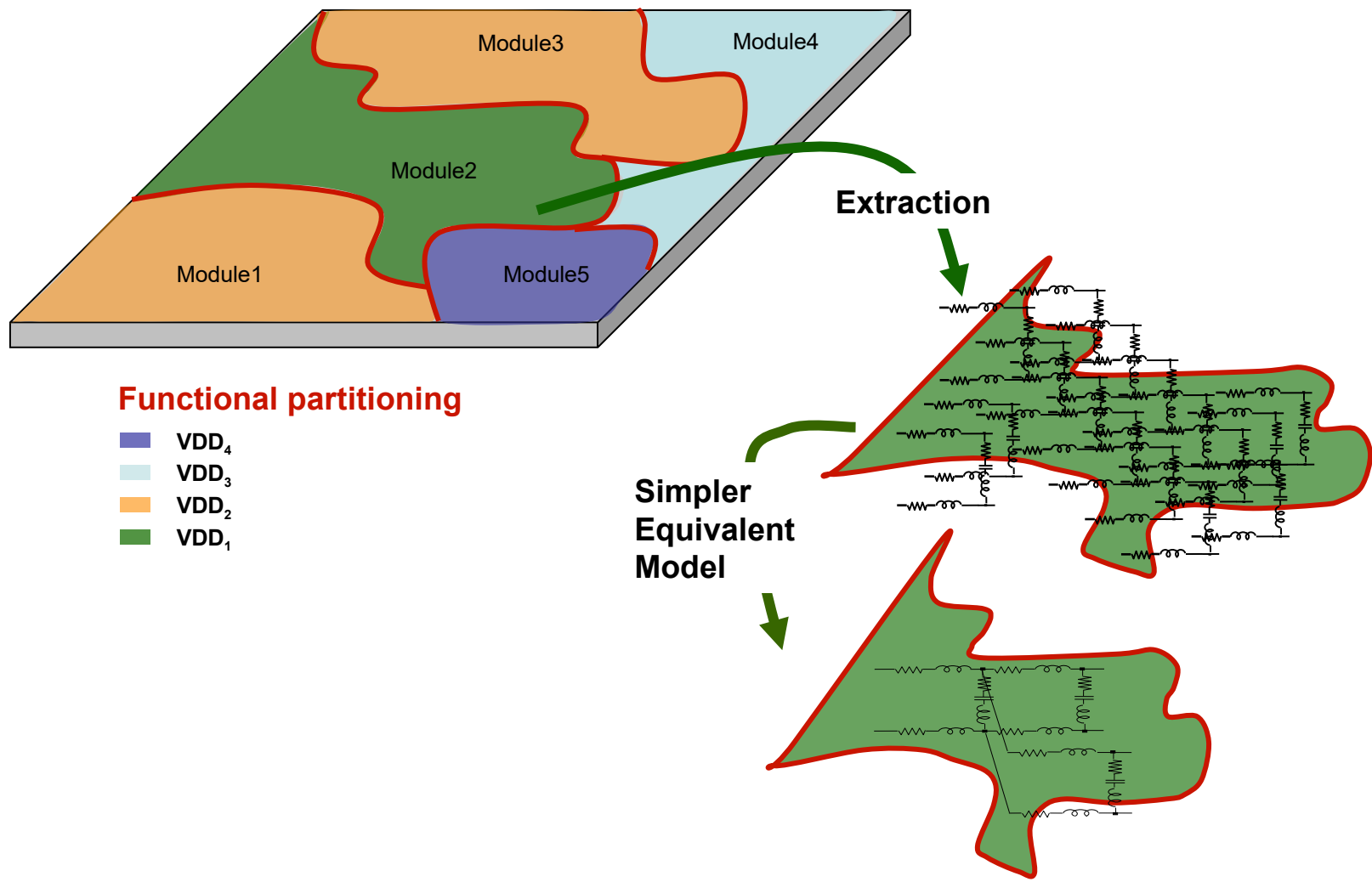
# Model Partitioning of a Power Distribution System


 
# Model of a Power Distribution System with n Modules




The same methodologies may be applied to larger structures

# AGENDA

- 1- Bandwidth of Interest
- 2- Model of a Power Distribution System
- 3- Bypassing Examples
- 4- Bypassing Methods
- 5- IC and PCB Designers Point of View
- 6- Power Distribution System Model Extraction
- 7- **Conclusion**
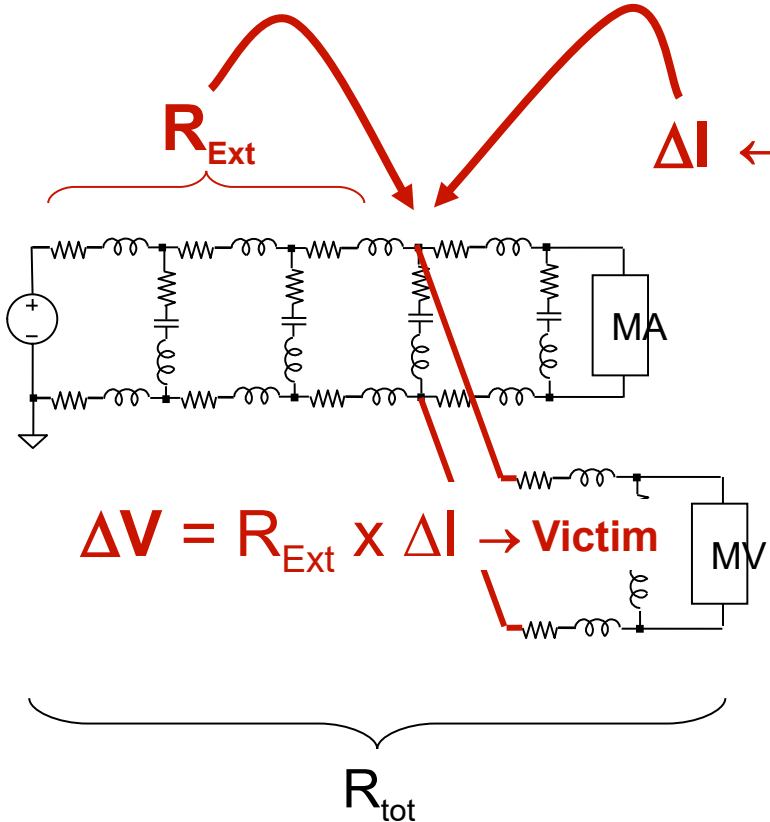
# Conclusion: Bypassing and Decoupling are **Essential**



$R_{tot} = R_{Ext} + R_{IC}$

A good bypassing does improve the decoupling.

Lowering  $R_{Ext}$  improves the decoupling of the system.

Best decoupling is obtained with low  $R_{Ext}$ .

Bypassing constrains  $R_{tot}$        $R_{tot}$  *small*

Decoupling constrains  $R_{Ext}$        $R_{Ext}$  *small*



# A Few References

- [PDN\_04] Power Distribution Networks in High Speed Integrated Circuits  
Andrey V. Mezhiba, Eby G. Friedman, 2004 by Kluwer Academic Publishers
- [Fujitsu\_02] Yoshihiko Imanaka, Takeshi Shioga, John D. Baniecki,  
Decoupling Capacitor with Low Inductance for High Frequency Digital Applications  
Fujitsu Sci. Tech. J., 38,1,p22-30 June 2002
- [Free\_06] Microprocessor Design Forum ISSCC 2006, Multi-Core Architectures, Designs and  
Implementation Challenges  
Presentation of D. Bouvier, Freescale, challenge of High Performance Multi-Core  
Processors for embedded Infrastructure
- [SPI\_05] CEI-Europe Course on Signal and Power Integrity of High Speed System Design  
Dr Istvan Novak, November 2005